# Relaxation Oscillator and One-Shot Using 555 Timer

Physics 116B Lab 11

Rev. 2, January, 2003

### Introduction

In this experiment you will use an FET version of a 555 timer (TLC555) to

- make a relaxation oscillator (astable multivibrator)
- use the circuit with a thermistor as the timing resistor to make a digital thermometer of sorts (example of telemetry and analog-to-digital conversion) and
- make a one-shot circuit (monostable multivibrator or timer).

### **Relaxation Oscillator**

Wire the circuit shown in Fig. 1. Note: black dots indicate connections. Lines crossing at right angles without black dots are not connected. Be sure to use a capacitor with a 10% tolerance for the 0.047  $\mu$ F timing capacitor. Use a 10 k $\Omega$  resistor for the timing resistor initially. Note that the output is connected to the trigger and threshold inputs through the timing resistor. Examine the circuit and convince yourself that the trigger/threshold level will vary between 1/3 and 2/3 of the supply voltage as the output switches from 0 V to a voltage close to the supply voltage and back. Observe (and copy in your report) the waveforms on the trigger/threshold node and on the output. Record the actual transition voltages at the trigger/threshold input and the high state output voltage. From these measurements and your analysis of the circuit, estimate the period of oscillation. Measure the oscillation frequency using the frequency counter in the Tektronix function generator and compare with what you expect.

#### **Digital Thermometer**

Now replace the  $10 \text{ k}\Omega$  timing resistor with the thermistor. This is a semiconductor device whose resistance varies with temperature in a known way. The oscillator frequency readout will now be a measure of the thermistor temperature. You will observe the frequency to increase if you press the thermistor between your fingers. Based on the supplied resistance vs. temperature chart, make a chart of expected oscillator frequency for temperatures between 0 and 50 degrees Celsius (in 5 degree steps). If the frequency were read into a computer, it would be simple to convert it to Celsius for display or recording.

## **One-Shot**

This circuit (Fig. 2) produces a pulse of known length following a short trigger. The transistor RC circuit is used to invert and stretch the input pulse to provide an appropriate trigger for the timer.

Use the pulse generator to produce a 5 V input pulse of approximately 10  $\mu$ s width at a spacing of 100 ms. Observe the pulse on the trigger input of the timer and sketch it to include in your report. Observe the operation of the timer circuit for timing resistances of 100 k $\Omega$  and 1.0 M $\Omega$ . Measure the periods. Analyze the operation of the circuit and compare the measured periods from what you expect from the analysis.

| Temperature<br>in celsius            | Kilohms                                   |   |
|--------------------------------------|---|---|
| -50*<br>-45*<br>-40*<br>-35*<br>-30* | 329.2<br>247.5<br>188.4<br>144.0<br>111.3 | + s V   |
| -25*<br>-20*<br>-15*<br>-10*<br>-5*  | 86.39<br>67.74<br>53.39<br>42.45<br>33.89 | R (IOKS2 or thermistor)   |
| 0*<br>5*<br>10*<br>15*<br>20*        | 27.28<br>22.05<br>17.96<br>14.68<br>12.09 | 8 4<br>2 TRIC KT7   |
| 25*<br>30*<br>35*<br>40*<br>45*      | 10.00<br>8.313<br>6.941<br>5.828<br>4.912 | 6 THR OUT 3 OUT   |
| 50*<br>55°<br>60*<br>65*<br>70*      | 4.161<br>3.537<br>3.021<br>2.589<br>2.229 | $\begin{array}{c} C \\ \cdot 047 \\ \pm 107 \\ \end{array} = \begin{array}{c} TLC \\ 555 \\ \end{array} $ |
| 75*<br>80*<br>85*<br>90*<br>95*      | 1 924<br>1.669<br>1.451<br>1.366<br>1.108 | ±10% = 555 + .014F  |
| 100°<br>105-<br>110°                 | 9735<br>6575<br>7579                      |   |
| Therm                                | nistor                                    |   |

I hermistor resistance

**Relaxation Oscillator** 

Figure 1: Relaxation oscillator diagram with thermistor resistance chart.

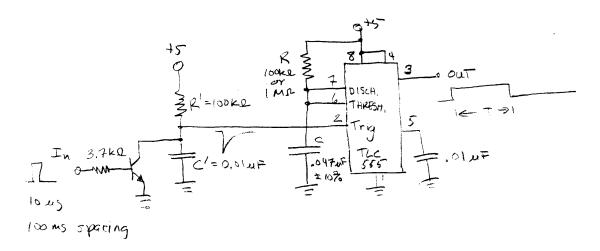


Figure 2: One-shot (timer) circuit.

| Operating Characteristics, VDD = 5V<br><u>PARAMETER</u> TEST CONDITIONS <u>MIN TYP MAX UNIT</u><br>Imma entored VDD = 5V to 15 V                                  |   | $(1K.100K) \xrightarrow{(6)}{C1} THES \xrightarrow{(0)}{TRIC} \xrightarrow{(0)}{C1} TRIC \xrightarrow{(1)}{TRIC} $ | RADIO SHACK, A DIVISION OF TANDY CORPORATION<br>U.S.A.: FORT WORTH, TEXAS 76102<br>CANADA: BARPIE, ONTARIO L4M 4W5<br>TANDY CORPORATION<br>MARTALA<br>MARTALA<br>AND PARE NOUSTRIL OF MANIME<br>BUSTON PARE NOUSTRIL OF MANIME |
|---|---|--|--|
| efectricial characteriatics at 25 C free-air temperature. VDD = 5<br>V to 15 V (unless otherwise noted)<br>PARAMETER TEST CONDITIONS MIN TYP MAX OWN<br>Thereford | 2 anonyce mere a<br>currenter<br>Derection 66 7/s 66 7/s   2 monoting of<br>Derection 100 - 5 V 100 pA   2 monoting of<br>Derection 100 - 5 V 100 pA   2 monoting of<br>Derection 100 - 5 V 100 pA   Pager current<br>Mager current<br>Supply verifier 100 pA 100 pA   Pager current<br>Mager curren   | 5 2  | RADIO SHACK, A DIVISI<br>U.S.A.: FORT W<br>CANADA: BARR<br>TANDY C<br>405194,00<br>31 VURBUOR PAG  |
| Radio Jack Catalog Number 276-1718<br>TECHNICAL DATA  | Tric of view<br>Tric of view<br>UUT of the post<br>Neteral biot again<br>Neteral biot again<br>N          | EURCION JABLE   FESET THORGEN LABLE   FESET THORGEN LABLE   UCMGE VOLVAGE VOLVAGE   USD VOLVAGE VOLVAGE   USD VOLVAGE VOLVAGE   USD VOLVAGE VOLVAGE   USD VOLVAGE VOLVAGE   Hann Low OIN   Hann Low OIN   Hann Low OIN   Hann Colson 23 YOD Low OIN   Hann Z 3 YOD As prevously estatisted OIN   Youtage levels from are norminal. As prevously estatisted OIN   Supply voltage. Voltage levels are norminal. Supply voltage. OIN   Supply voltage levels are norminal. Supply voltage levels are norminal. OIN OIN OIN   Supply voltage levels are norminal. Supply voltage levels are norminal. OIN OIN OIN OIN   Supply voltage levels are norminal. Supply voltage levels are norminal. OIN OIN OIN OIN </td <td></td>   |  |
| Radio Mac<br>TECHNICAL D  | <b>1LC555 Timer</b><br><b>Features</b><br><b>Features</b><br>Very Low Power Consumption<br>Term Typar 2019 = 50 V<br>capable of Very High-Speed Opera-<br>tion Typically 2 mHz in Astable<br>Mode<br>Complementary CMOS output Cap<br>and a pail on the<br>and a pail on the a pail on the<br>and a pail on the a pail on the a pail on the a pail on the<br>and a pail on the a pa | Description<br>The TLC555 is a monolink timing circuit fabricated using the Lin-<br>CMOS <sup>2</sup> process. Due on the high-impedance moust typically (0.2<br>20) is in copasition to the high-impedance moust typically (0.2<br>20) is in copasition to the high-impedance moust typically (0.2<br>20) is in copasition to the high-impedance moust typically (0.2<br>20) is in copasition to the high-impedance moust typically (0.2<br>20) is in copasition to the high-impedance moust typically (0.2<br>20) is in copasition to the high-impedance moust typically (0.2<br>20) is the high-impedance moust the impedance<br>the transformation of the high-impedance moust the high-<br>center and one categories of the 2 bit and is the transformation<br>of the transformation of the transformation of the<br>transformation of the categories of the 2 bit and is the compatibility<br>of the the MESS, the threshold and trigger levels are normaly two<br>trigger level. The high-top as a due range of supply voltage<br>signal from 2 outs to 18 outs.<br>The the MESS for the threshold and trigger levels are normaly two<br>trigger level, the the high-top as a due to the threshold level<br>by use of the control voltage terminal. When the trigger input taits<br>the trigger input taits down the high-top as due to the<br>trigger input taits down the high-top as due to the<br>power trigger input taits the trigger level the threshold level<br>to the trigger level. When the rest input gas high the<br>trigger input taits down the high-top as the trinshold level<br>to the trager input taits down the high-top as the trinshold level<br>to the trager input taits down the high-top as the trigger<br>bound the cutoru types (on Whenever the cutoru types (on<br>the top out) at out.   | While the complementary CMOS output is capable of sixting over<br>100m and sourcing over 10 md, in the TLC5656 suiths gravity re-<br>outed supply current spikes during output transitions. This minimizas<br>the need for the large decoupling capacitors required by the NE555.<br><i>LinckUOS</i> is a trademark for a silicongate IC process by Texas<br>Instruments.  |

Figure 3: TLC555 specifications.