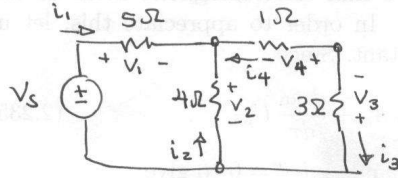


M 08-OCT-2007

PHYSICS 116A HW#1

CH1: 8, 12, 18 ; CH2: 6, 8, 30, 47, 48, 59

1-8



~~GIVEN $V_1 = 30V$~~

a) Given $V_1 = 30V$; find i_1

$$V_1 = i_1 R_1 \Rightarrow 30V = i_1 (5\Omega) \Rightarrow \boxed{i_1 = 6A}$$

b) Given $V_2 = 12V$; find i_2

$$i_2 = -V_2 / R_2 = -12V / 4\Omega \Rightarrow \boxed{i_2 = -3A}$$


c) Given $V_2 = -9V$; find i_3

$$i_3 = -V_3 / 3\Omega = -(-9V) / 3\Omega \Rightarrow \boxed{i_3 = +3A}$$

d) Given $V_4 = -3V$; find i_4

$$i_4 = V_4 / R_4 = -3V / 1\Omega \Rightarrow \boxed{i_4 = -3A}$$

1.12

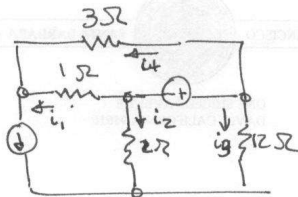a) Given $i_1 = -4A$; find v_1

$$v_1 = -i_1 R_1 = -(-4A)(1\Omega) \Rightarrow v_1 = +4V$$

b) Given $i_2 = 1A$; find v_2


$$v_2 = i_2 R_2 = (1A)(2\Omega) \Rightarrow v_2 = 2V$$

c) Given $i_3 = 1A$; find v_3

$$v_3 = -i_3 R_3 = -(1A)(12\Omega) \Rightarrow v_3 = -12V$$

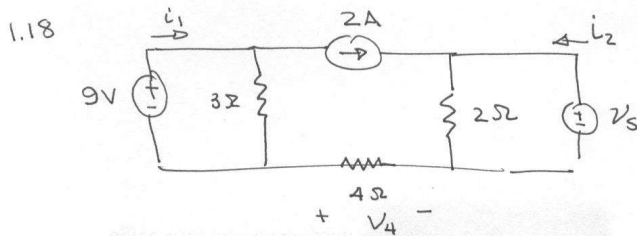d) Given $i_4 = 2A$; find v_4


$$v_4 = i_4 R_4 = (2A)(3\Omega) \Rightarrow v_4 = +6V$$






Find V_4 for $V_s = 2, 4, 6V$

This is a perfect superposition problem:

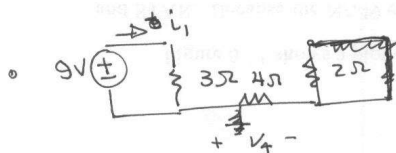lets consider ~~each~~ each source independently:




V_4 from the 9V = 0

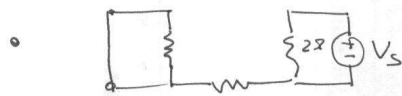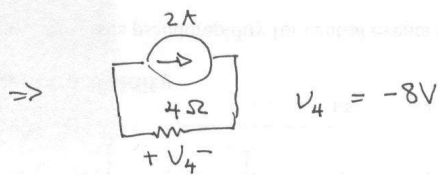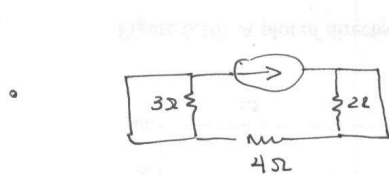

⇒ V_s only effects the current through the 2Ω.

⇒ for all values of V_s , $V_4 = -8V$

2.6

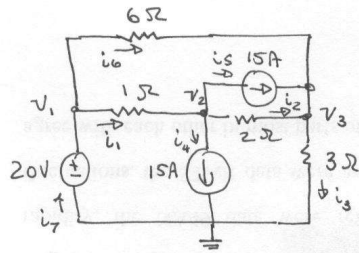Find v_1, v_2, v_3

$$v_1 = 20V$$

by KCL @ node v_2

$$\frac{v_2 - 20}{1\Omega} + 15 + 15 + \frac{v_2 - v_3}{2\Omega} = 0$$

$$2v_2 - 40 + 60 + v_2 - v_3 = 0$$

$$3v_2 - v_3 = -20$$

eq 1

KCL @ node v_3

$$15 = \frac{v_3 - 20}{6} + \frac{v_3 - v_2}{2} + \frac{v_3}{3}$$

$$90 = v_3 - 20 + 3v_3 - 3v_2 + 2v_3$$

$$-3v_2 + 6v_3 = 110$$

eq 2

2 Eqs

2 unknowns

Add eq 1 + eq 2

$$5v_3 = 90 \Rightarrow v_3 = 18V$$


USE EQ 1:

$$3v_2 - 18 = -20$$


$$3v_2 = -2$$

$$v_2 = -2/3$$

2.59

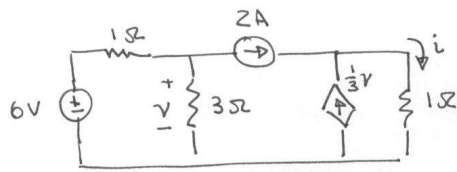

a) Find i and v due to 6V source

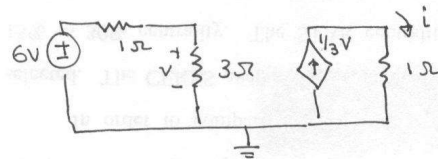


current source becomes open

~~$v = \frac{6V}{3\Omega} = 2A$~~

Voltage divider: $v = \frac{3}{4}(6V) = \boxed{4.5V}$

$i = \frac{1}{3}v = \boxed{1.5A}$

b) Find i and v due to 2A source

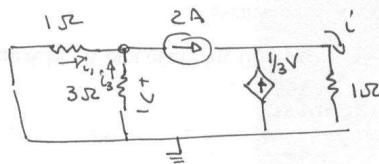

voltage source becomes short

i_1 and i_3 are a current divider of 2A

$i_3 = \frac{R_1}{R_1 + R_3} I = \frac{1}{4}(2A) = 0.5A$


$v = (-0.5A)(3\Omega) = \boxed{-1.5V}$

$i = 2A + \frac{1}{3}(-1.5V) = 2A - 0.5A = \boxed{1.5A}$

c) $v_{TOT} = 4.5 - 1.5 = \boxed{3.0V}$

$i_{TOT} = 1.5 + 1.5 = \boxed{3.0A}$

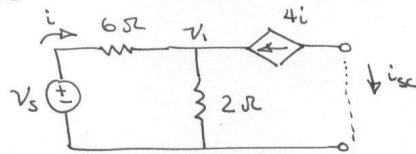2.47 Demonstrate that the Norton Equivalent




First find the I_{eq} , which is the short circuit current

$$\text{KCL @ } v_1, \quad i + 4i = \frac{v_1}{2} \Rightarrow 5i = \frac{v_1}{2} \Rightarrow 5\left(\frac{v_s - v_1}{6}\right) = \frac{v_1}{2}$$

$$5v_s - 5v_1 = 3v_1 \Rightarrow 5v_s = 8v_1 \Rightarrow v_1 = \frac{5}{8}v_s$$

$$i_{sc} = -4i = -4\left(\frac{v_s - v_1}{6}\right) = -4\left(\frac{v_s - \frac{5}{8}v_s}{6}\right) = -4\left(\frac{\frac{3}{8}v_s}{6}\right) = \boxed{\frac{-v_s}{4}}$$

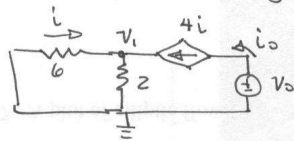Next, find R_{eq} by putting v_0 across the load



$$\text{KCL @ } v_1: \quad i + 4i = \frac{v_1}{2} \Rightarrow 5i = \frac{v_1}{2} \Rightarrow 5\left(\frac{-v_1}{6}\right) = \frac{v_1}{2}$$


$$-5v_1 - 3v_1 = 0 \Rightarrow v_1 = 0$$

$$\Rightarrow i = 0$$


$$\Rightarrow i_0 = 0$$

$$R_{eq} = \frac{v_0}{i_0} = \frac{v_0}{0} = \infty$$

Norton Equivalent:

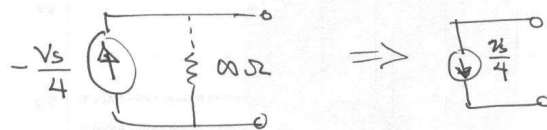

2.48

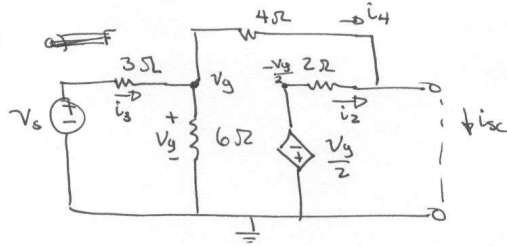


(a) Find the Norton Equivalent

First find i_{sc} : $i_{sc} = i_2 + i_4$

$$i_{sc} = \left(\frac{-V_g/2}{2} \right) + \frac{V_g}{4} = -\frac{V_g}{4} + \frac{V_g}{4} = \boxed{0}$$

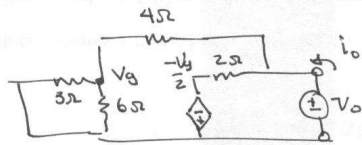Next, consider V_o at the load to determine R_{eq}



consider $3\Omega \parallel 6\Omega \Rightarrow R_{11} = \frac{(3)(6)}{3+6} = 2\Omega$



get V_g from voltage division $\Rightarrow V_g = \frac{2}{2+4} V_o = \frac{1}{3} V_o$

get i_o from KCL @ V_o


$$i_o = \cancel{\frac{V_g V_o}{2}} - (i_4 + i_2) = -\left(\frac{V_g - V_o}{4} + \left(\frac{-V_g/2 - V_o}{2} \right) \right)$$

$$i_o = -\left(\frac{V_g}{4} - \frac{V_o}{4} - \frac{V_g}{4} - \frac{V_o}{2} \right) = + \frac{3V_o}{4}$$
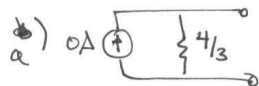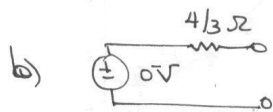
$$R_{eq} = \frac{V_o}{i_o} = \frac{V_o}{\frac{3}{4}V_o} = \boxed{\frac{4}{3}\Omega}$$



2.28

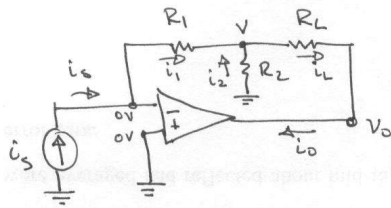

Find a) V_o
b) i_o

$$\text{KCL @ node } V: i_1 + i_2 = i_L = i_o$$

$$-\frac{V}{R_1} - \frac{V}{R_2} = \frac{V - V_o}{R_L} = i_o$$

$$i_1 = i_s = -\frac{V}{R_1} \Rightarrow V = -i_s R_1$$

$$i_s + i_s \frac{R_1}{R_2} = i_o \Rightarrow i_o = \left(\frac{R_2 + R_1}{R_2} \right) i_s$$

$$\frac{V - V_o}{R_L} = i_o \Rightarrow \frac{-i_s R_1 - V_o}{R_L} = i_o$$


$$-i_s R_1 - V_o = i_o R_L$$

$$V_o = -i_s R_1 - i_o R_L$$

$$V_o = -i_s R_1 - \left(\frac{R_2 + R_1}{R_2} \right) R_L i_s$$

$$\text{a) } \boxed{V_o = - \left(R_1 + R_L + \frac{R_1 R_L}{R_2} \right) i_s}$$

2.30

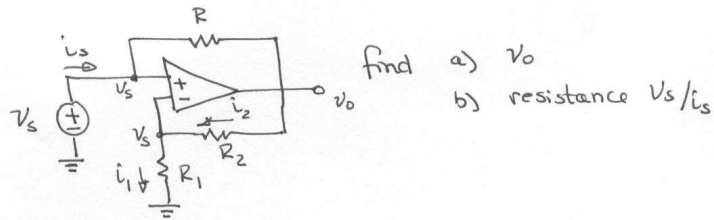

find a) v_o
b) resistance v_s/i_s

$$i_2 = i_1 \Rightarrow \frac{v_o - v_s}{R_2} = \frac{v_s}{R_1}$$

$$v_o - v_s = \frac{R_2}{R_1} v_s$$

$$v_o = \frac{R_2}{R_1} v_s + v_s = \left(\frac{R_2 + R_1}{R_1} \right) v_s$$

$$\begin{aligned} \text{b) } i_s &= \frac{v_s - v_o}{R} = \frac{v_s}{R} - \frac{1}{R} \left(\frac{R_2 + R_1}{R_1} \right) v_s \\ &= \frac{v_s}{R} - \frac{R_2}{R R_1} v_s - \frac{v_s}{R} = -\frac{R_2}{R R_1} v_s \end{aligned}$$

$$\boxed{\frac{v_s}{i_s} = -\frac{R R_1}{R_2}}$$