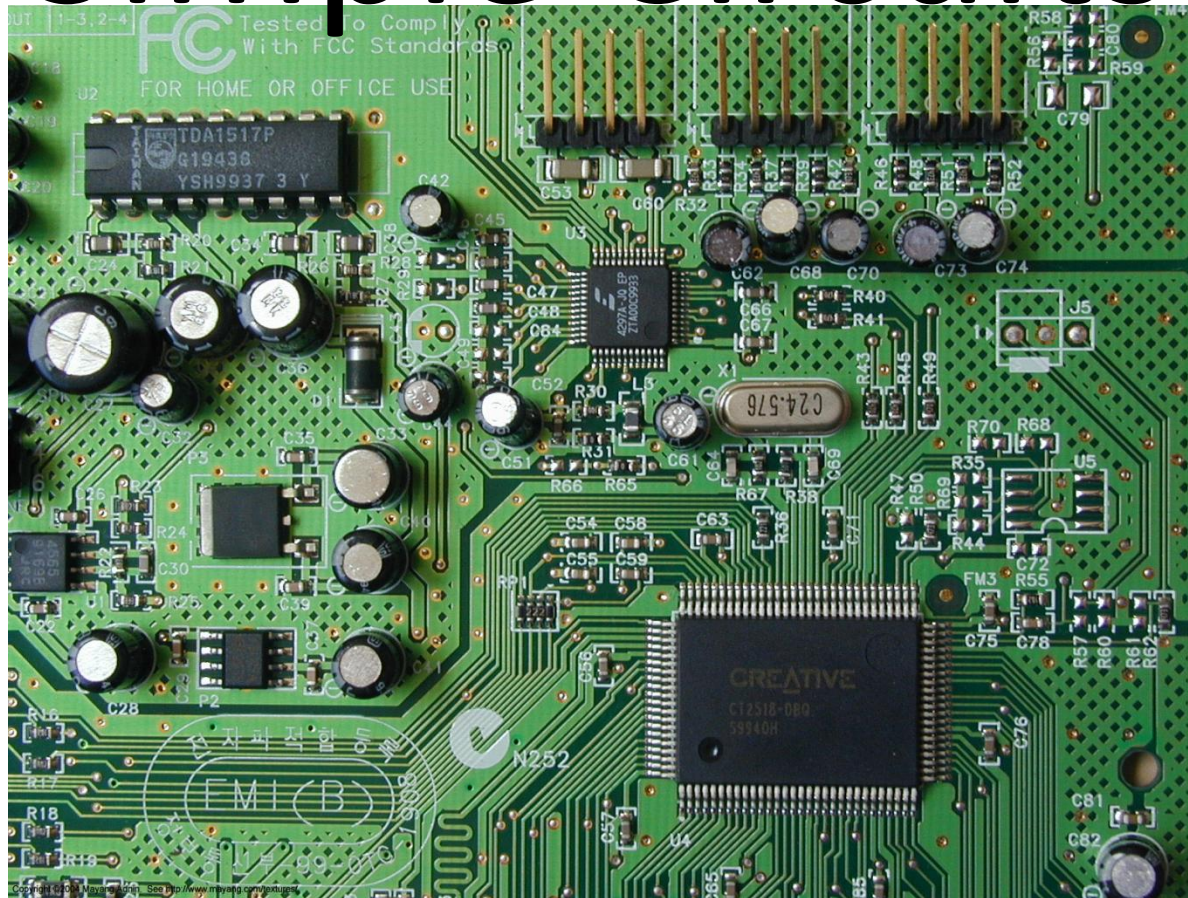


Simple Circuits



Conservation of Energy Density

In the First lecture, we started with energy conservation. We divided by volume (making conservation *intensive* rather than *extensive*) to get an energy density conservation equation.


For the non-isolated system, we added in pumps and resistance from the pipes to get a more general equation which describes the general features of fluid systems:

$$\frac{\sum \Delta E_{\text{External}}}{V} = \frac{E_{\text{Pump}}}{V} - \mathbf{IR} \quad \Rightarrow \quad \Delta P + \rho g \Delta y + \frac{1}{2} \rho \Delta(v^2) = \frac{E_{\text{Pump}}}{V} - \mathbf{IR}$$

In this lecture, instead of dividing by volume, we will divide the energy by the electric charge. This again gives us an intensive energy density equation which now describes the behavior of electrical circuits.

Comparison of Fluids to Electricity

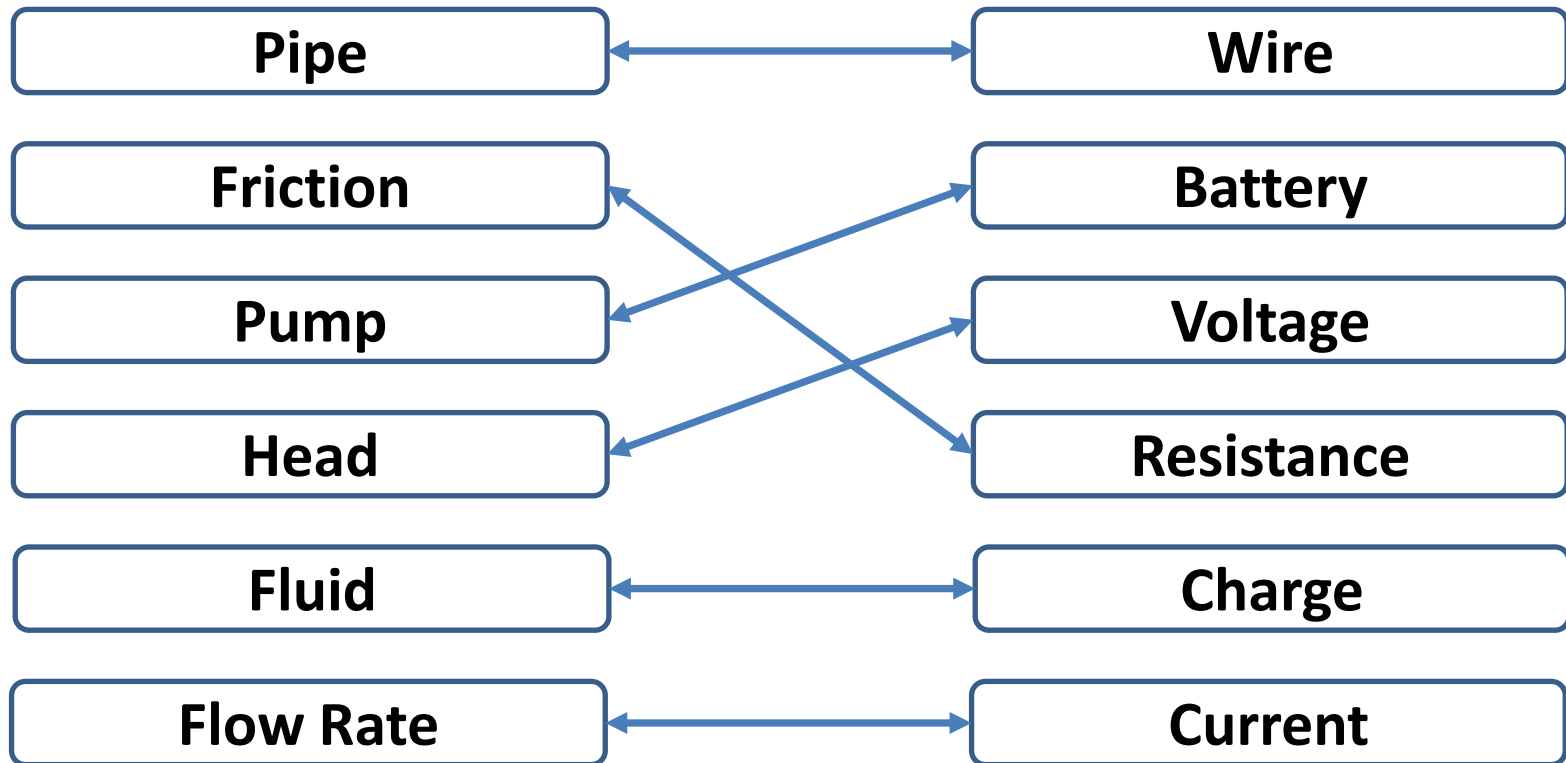- Fluid systems and electrical circuits are analogous:



Units of Electrical Circuits

Quantity	Unit	Definition	Dimensions
Electric Charge (q)	<i>Coulomb</i> (C)	$1 e = 1.6 \times 10^{-19} \text{ C}$	1 C
Energy (E)	<i>Joule</i> (J)	1 Nm	$1 \text{ kg m}^2 / \text{s}^2$
Electric Potential (V)	<i>Volt</i> (V)	$1 \text{ V} = 1 \text{ J/C}$	$1 \text{ kg m}^2 / \text{s}^2 \text{ C}$
Electric Resistance (R)	<i>Ohm</i> (Ω)	$1 \Omega = 1 \text{ V/A}$	$1 \text{ kg m}^2 / \text{sC}^2$
Electric Current (I)	<i>Ampere</i> (A)	$1 \text{ A} = 1 \text{ C/s}$	1 C/s
Power (P)	<i>Watt</i> (W)	$1 \text{ W} = 1 \text{ J/s}$	$1 \text{ kg m}^2 / \text{s}^3$
Energy (E)	<i>kiloWatt-Hour</i> (kW-hr)	$3.6 \times 10^6 \text{ J}$	

What is a Circuit?

An electrical device that provides a path for electrical current to flow


Conservation of charge requires that the circuit must be **complete**, i.e. it must be continuous.

A circuit that does not have a complete conducting path is said to be an **open circuit**.

In the diagram at the right, the switch *opens* the circuit.


A component can be in a condition where the current has alternative and lower resistance conducting path. This is known as a **short circuit**.

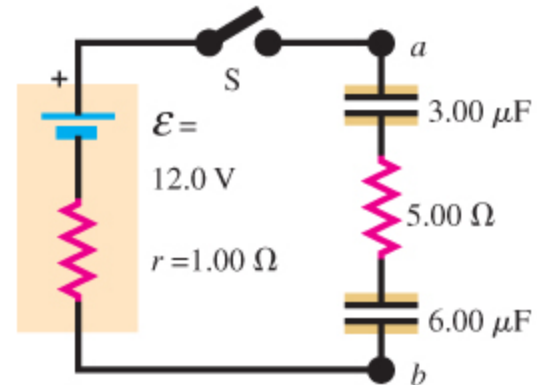Often a circuit will connect to **ground**. Ground is the reference voltage defined as the electric potential of the surface of the earth.




DEMO: Circuit Board

Circuit Components and Symbols

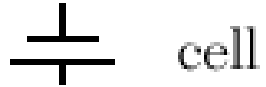

cell

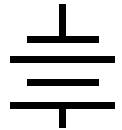A cell maintains a defined voltage across its two terminals



battery

A battery is a collection of two or more cells



switch

A switch can be set to open or close the circuit



voltmeter

A voltmeter measures the potential between two points



ammeter

An ammeter measures the current flowing through it



resistor

A resistor impedes the flow of current



variable resistor

A variable resistor has an adjustable resistance



lamp

A lamp is a resistor that produces light

Electric Energy per Charge -- Voltage

- **Voltage:** Electrical potential energy per unit charge.
- In fluid systems:

$$\Delta Head = \frac{E_{Pump}}{V} - IR$$

- In electrical circuits:

$$\Delta Voltage = \varepsilon - IR$$

Definition of a Resistor

- **Resistor:** Any circuit component that
 1. Opposes current
 2. Produces a voltage drop
 3. $\Delta V \propto I \implies V = IR$
- Resistors use/dissipate power:

$$P = I\Delta V$$

DEMO: Resistor Model

A conductor with zero resistance is a wire



Batteries and Power Supplies

Batteries, generators, or power supplies are able to maintain a defined electric voltage (energy per charge) across its two terminals. To do this, these devices must convert energy from some other form.

Batteries use chemical energy (E_{bond}) and convert this to electric energy.

Generators convert mechanical energy.

Power supplies convert the AC line power into another form of electric Energy.

Batteries have a characteristic electromotive force (\mathcal{E}), measured in volts.




Meters



A **voltmeter** is an instrument used for measuring the electrical potential difference between two points in an electric circuit.

An **ammeter** measures the electric current flowing through its leads.

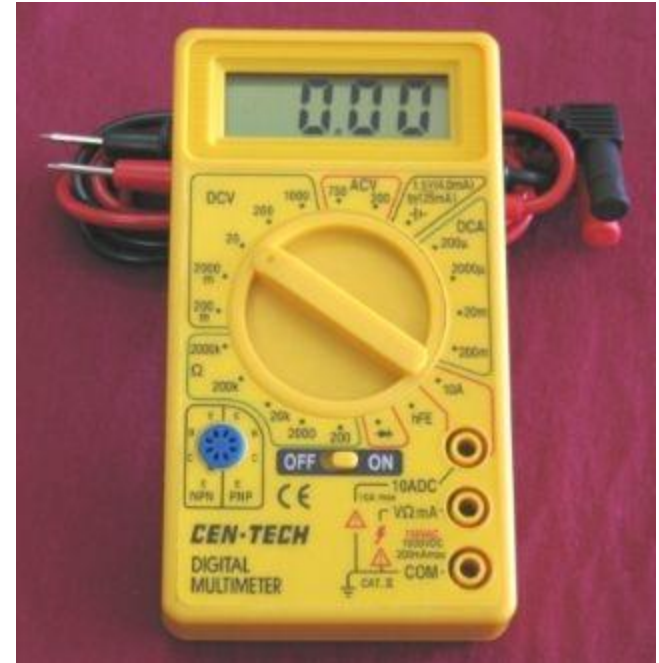An **ohmmeter** uses a battery to run a small current through an unknown resistor. By measuring the battery voltage and the current and using Ohm's Law, the device determines the resistance.



Ohm's Law ($V = IR$)

In electrical circuits, **Ohm's law** states that the current through a component between two points is directly proportional to the potential difference or voltage across the two points, and inversely proportional to the resistance between them.

$$I = \frac{V}{R}$$

DEMO: Single Resistor
and Meters

Electrical Power

In resistive circuits, electrical power is calculated using Joule's law:

$$P = V \cdot I$$

where P is the electric power, V the potential difference, and I the electric current.

In the case of resistive (Ohmic, or linear) loads, Joule's law can be combined with Ohm's law ($I = V/R$) to produce alternative expressions for the dissipated power:

$$P = I^2 R \qquad P = \frac{V^2}{R},$$



DEMO: Single Light Bulb

Capacitor

- **Capacitor:** Any circuit component that
 1. Stores charge
 2. Produces a voltage drop
 3. $\Delta V \propto Q$
- Capacitors can behave like rechargeable batteries




Series Circuits

A series circuit is one in which there is only a single conducting path. There are no branches and all components come one after another.

The current will flow around the circuit from the positive to the negative terminal of the battery.

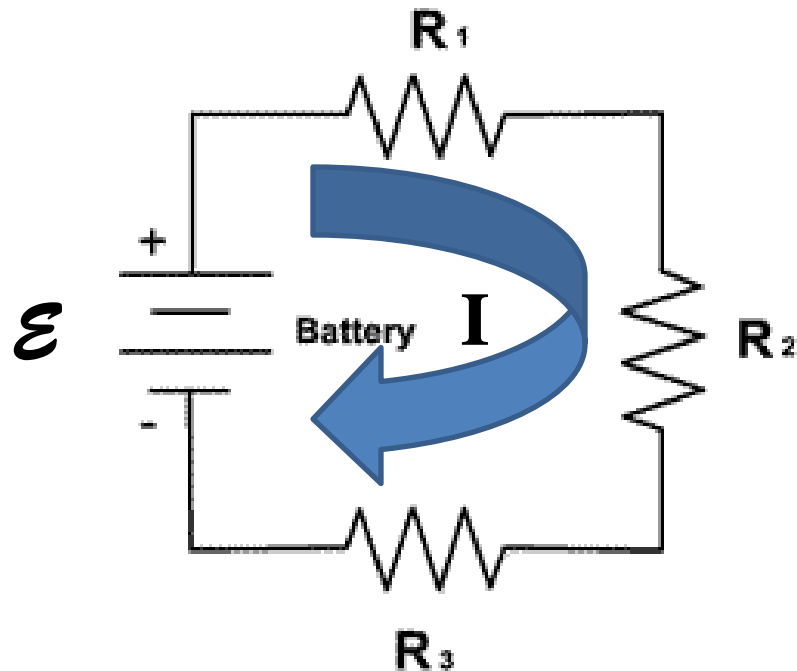
All the components will experience the same current, however each will have a voltage drop determined by the size of its resistor.



$$\mathcal{E} = IR_1 + IR_2 + IR_3$$

The Loop Rule

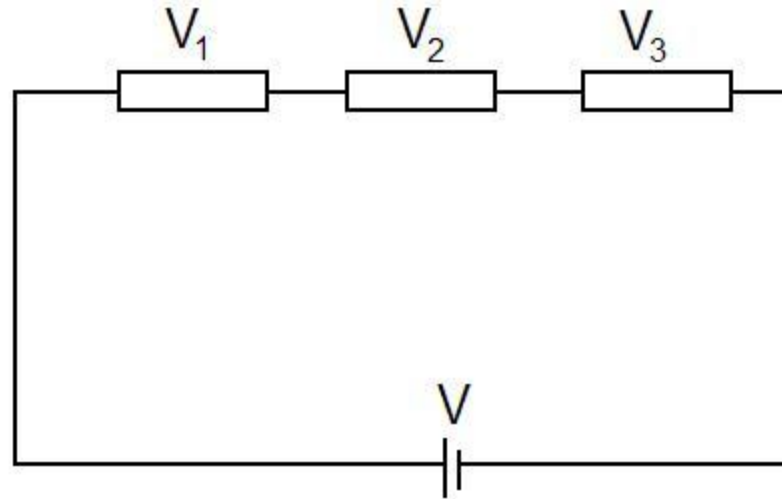For any closed loop that one can draw on a circuit, no matter how complex, the sum of the voltage drops must be equal to the sum of the voltage rises (forward biased batteries).




$$\sum \mathcal{E} = \sum I R_i$$

$$V = V_1 + V_2 + V_3$$

Conservation of energy

Simple Flow Exercise

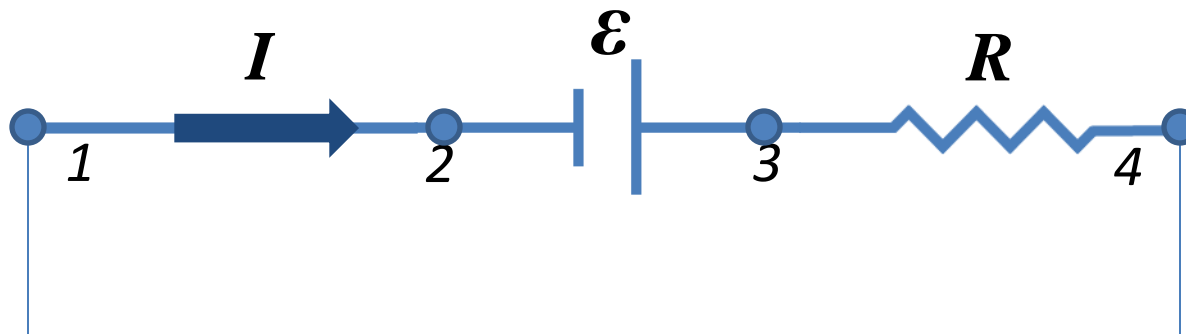- Suppose current I flows through point 1 and consider a battery with emf ε and resistor with resistance R .
 - Calculate the current through point 2, 3 and 4.
 - Calculate voltage change between points 1&2, 2&3 and 3&4.
 - Calculate power used/dissipated by resistor.




Parallel Circuits

A parallel circuit is one in which the leads of the components are joined by a common wire which is then connected across the battery or other voltage source.

The current will be split between the parallel components, however they will all have the same voltage drop.


$$V = I_1 R_1 = I_2 R_2 = I_3 R_3$$

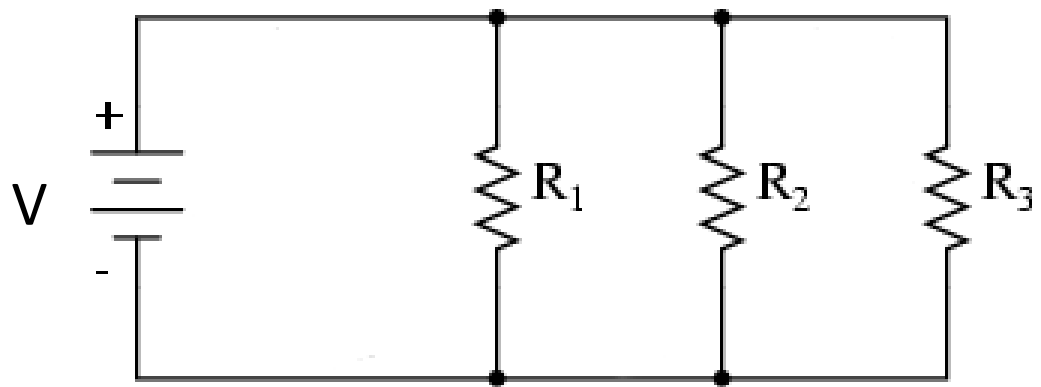

The Junction Rule

At any junction (or node), the sum of the incoming currents must be equal to the sum of the outgoing currents.



$$\sum I_{in} = \sum I_{out}$$

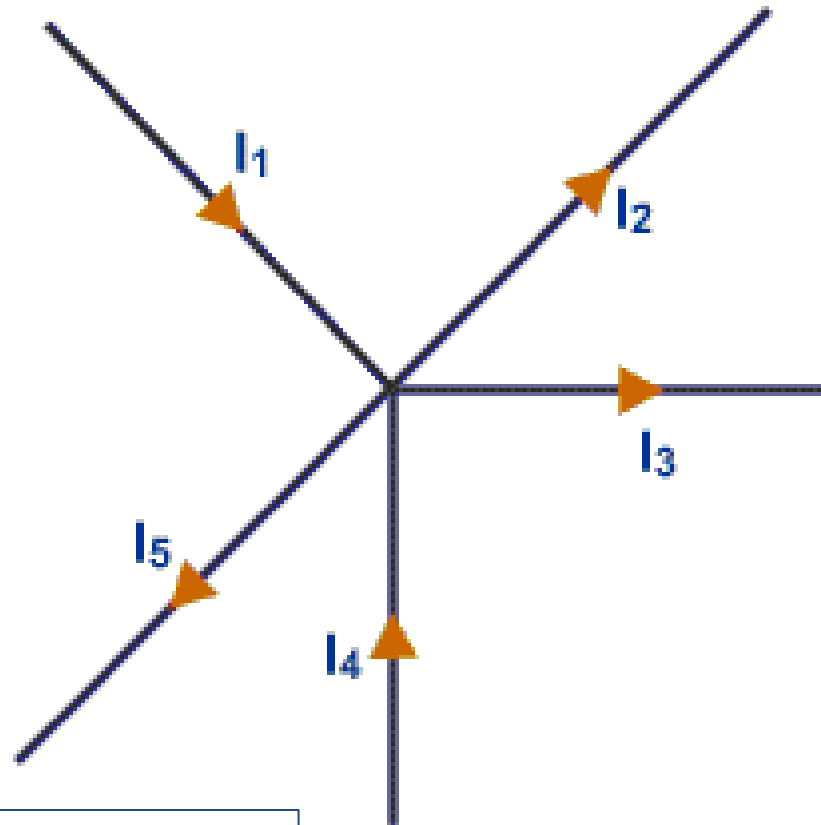

Conservation of charge

Series and Parallel

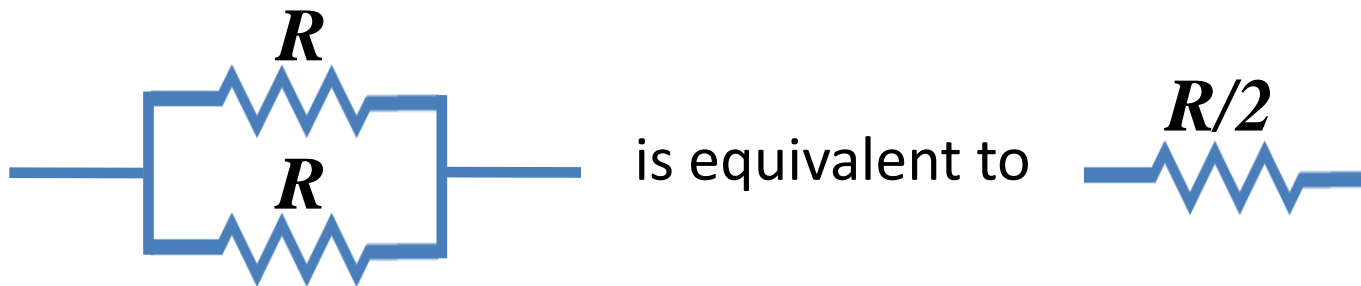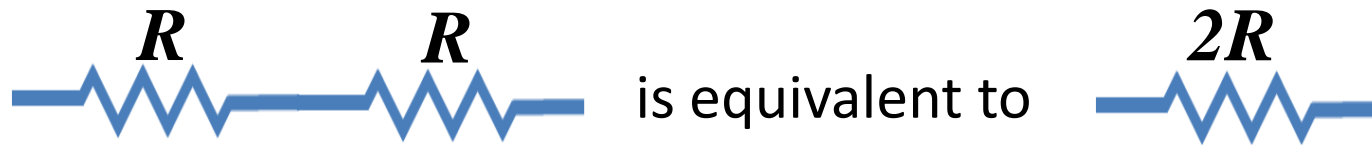- Complicated circuits can be simplified.



- Resistors in series:

$$R_{equiv} = R_1 + R_2 + R_3 + \dots$$

- Resistors in parallel:

$$R_{equiv} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \right)^{-1}$$

DEMO: Series Light Bulbs

Household Electrical Power



DEMO: Utility Box

Household power is delivered as AC power.

In the North America, standard electrical outlets have $110\text{ V}_{\text{rms}}$ at 60 Hz.

Much of the rest of the world uses 220 V at 50 Hz.

Transmission lines carry power from plants at several thousand volts. This is stepped down at a series using a series of transformers. The final stage is in your breaker box at the power meter. There is a center tapped transformer. Taking either lead to ground gets the 110 V. For more energy demanding appliances, one can wire both leads to get 220 V.

Announcements

Remember the MLK day Holiday.

Section 01 (Marcus) does not meet on Friday. No sections meet on Monday or Tuesday.

Death by Electricity

It's the current that kills not the voltage



